

5LIH0 Project Report : 16-bit Sklansky Adder

Burak Ergül(1280104)

Tamas Oliver Kocsis(1281887)

Keyshav Mor(1237978)

For the course : 5LIH0 Digital Integrated Circuit Design(Q2)

Department of Electrical Engineering

Eindhoven University Technology

Academic Year 2018-2019

I. INTRODUCTION

For the course 5LIH0: Digital Integrated Circuit Design at Eindhoven University of Technology, we have implemented a 16-bit Sklansky Adder.

The Sklansky Adder is a Tree Adder which are a family of Full Adders intended to reduce delays associated with Carry Look-Ahead, Carry-Bypass and Carry-Select Adders. These adders are used to make addition arithmetic circuits faster, consume lower power and area. However, for wide Adders where Number of Input Bits are greater or equal to 16, the delay of the Carry Look-Ahead, Carry-Bypass and Carry-Select adders increases as the Carry goes through the look ahead stages. This delay can be reduced by looking ahead across the look ahead blocks, which essentially gives rise to Tree Adders.

The Sklansky Adder is one such adder proposed by Jack Sklansky in his paper titled "Conditional-Sum Addition Logic" in the year 1960. The main advantage of the Sklansky Adder is that it has lower numbers of logic-levels and relatively easier routing which makes it a popular choice while implementing Tree Adders adding numbers greater than or equal to 16-bits.

II. PROBLEM FORMULATION

A. Objectives of the Project

The primary objective of the project is to understand CMOS VLSI Design Process for 45nm CMOS technology using the FreePDK45 process design kit in conjunction with Cadence Virtuoso Analog Design Environment. To achieve this objective, we implement a 16-bit Sklansky Adder. The design process included schematic drawing, drawing layout of the schematic and post-layout simulation in prescribed conditions. The final design must demonstrate 16-bit adding functionality during post-layout simulation.

B. Specifications of the Project

2 16-bit numbers A [A15:A0] and B [B15:B0] along with a Carry-Input signal CIN are inputs to the Adder. The power supply to the adder and all its individual components is 1 V. The adder is tested under two different loads: 10f Farad and 100f Farad.

The adder must be implemented with static CMOS circuits which could be fully complementary and may have pass transistors or transmission gates. The transistors used in the low-level design should be standard threshold voltage transistors. The design should be optimized for size, power-consumption and delay. The rise-time (10 % - 90 %) of output voltage swing and fall time (90 % - 10 %) of the

output voltage swing needs to be under 100 pico Seconds at a simulation temperature of 90° Celsius. Moreover, the circuit should function at input frequencies of 500 MHz or greater.

III. CMOS CIRCUIT DESIGN

A. 16-bit Sklansky Adder

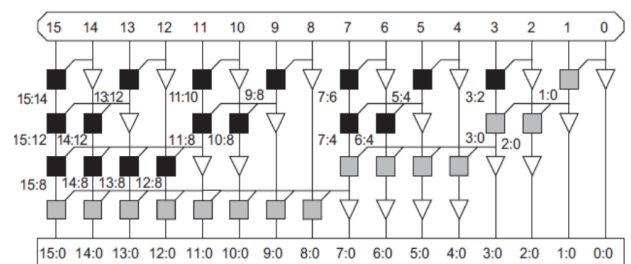


Fig. 1 The 16-bit Sklansky Adder PG Network

The 16-bit Sklansky Adder is a tree adder as we have mentioned previously. To understand the functioning of this adder, we need to understand the P(Propagate) and G(Generate) signals. The adder generates a carry when C_{out} is true independent of C_{in} , so $G = A \cdot B$. Whereas, the adder propagates a carry; i.e., it produces a carry-out if and only if it receives a carry-in, when exactly one input is true: $P = A \oplus B$. This carry generation and propagation is central to functioning of the adder.

We can generalize these signals to describe whether a group spanning bits i to j , inclusive, generate a carry or propagate a carry. A group of bits generates a carry if its carry-out is true independent of the carry-in; it propagates a carry if its carry-out is true when there is a carry-in.

These signals can be defined recursively for $i \geq k > j$ as

$$G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j} \dots \dots \dots (1)$$

$$P_{i:j} = P_{i:k} \cdot P_{k-1:j} \dots \dots \dots (2)$$

These two signals form the basic blocks of our 16-bit Sklansky Adder Schematic. The Sum for bit i can be then represented as

$$S_i = P_i \oplus C_{i-1} = P_i \oplus G_{i-1:0} \dots \dots \dots (3)$$

The adder consists of 3 building blocks, Black Cells, Gray Cells and Buffers. Black Cells generate and propagate logic to future stages. Gray cells generate logic and calculate sums which are ultimately used at the end. Buffers are used to ensure that the signal is propagated successfully to the

output to generate a full output voltage swing and minimize the load on critical paths.

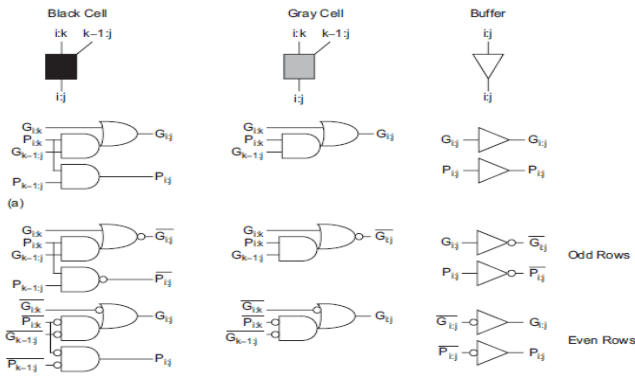


Fig.2 Black Cell, Gray Cell and Buffers

The critical path of this adder circuit is from the input point of Carry-in signal to the point where Carry-out signal is obtained along with the sum of input bits. This can be illustrated in Fig.1 by the concatenation of Gray cells from bit 0 till bit 15. The Sklansky Adder, with appropriate sizing reduces the delay on the critical path to

$$t_{tree} = t_{pg} + [\log_2 N]t_{AO} + t_{xor} \dots \dots \dots (4)$$

where t_{pg} is delay of propagate-generate cells, t_{AO} is delay of AND and OR gates in the gray cell and t_{xor} is the delay of XOR gates required for final summation.

B. Schematic of the Circuit

 


Fig. 3 Schematic of the 16-bit Sklansky Adder (LSB on the right, MSB on the left)

 


Fig.4 Interface of PG Logic, Black Cell and Gray Cells

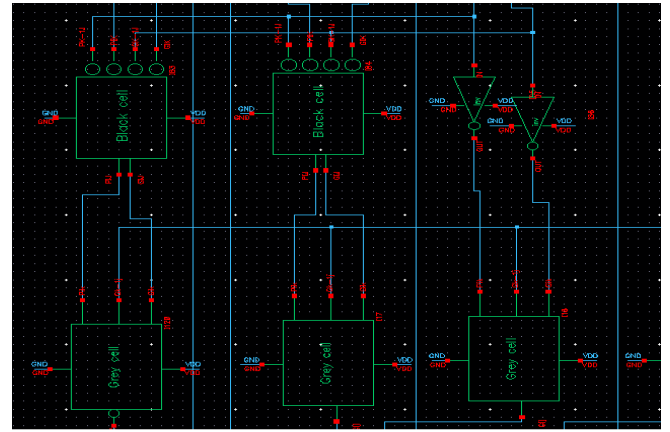


Fig.5 Interface of Black Cells (inverted inputs) with Gray Cell

 


Fig.6 Interface of Gray Cells with final summation XOR gates.

We chose to make a full complementary static CMOS design for all the aforementioned gates. Our design includes different versions of black and grey cells with either an inverted input, an inverted output or non-inverted ports such that each gate in the sequence complements the next with only a few inverters required. This design reduces the area and makes the overall design process easier.

The choice of design for the xor gate can be mentioned here as well since there are several designs that can be compared. The pass transistor logic design has 6 transistors but it doesn't have a full output voltage swing and so it requires a buffer at the output, which means 4 more transistors. The full complementary design requires 8 transistors and has a full output voltage swing although it also requires a buffer at the end to be able to drive the capacitive load. We chose to use the full complementary design since we thought it would be more robust and easier to design. However, in hindsight, the pass transistor logic design is smaller and would have been the better choice (considering it also has a full output voltage swing with a buffer at the output). The difference is two transistors per xor gate.

C. Sizing of Transistors

The sizing of transistors and gates is done along the critical path to achieve minimum propagation delay between the input signal and the output carry signal. For achieving this

goal, we used the inverter of NMOS width = 90nm, PMOS width = 145nm and Length = 50nm as our base reference.

We did the sizing of the critical path as per the stipulated output load capacitance of $C_{load}=100f$ Farad. With the help of the reference inverter we were able to figure out the Logical effort(g) of each gate along the critical path, which in turn gave us the logical effort along the whole path(G). Similarly, since we calculated the branching effort of gates along the path which gave us the combined Branching effort(B) along the whole path.

The challenging part was to figure out the input load capacitances of the CMOS gates at the PG Logic stage which was found through the Cadence Virtuoso software. These combined capacitances gave us the value of C_{in} , which in turn helped us figure out the Electrical effort F of the critical path ($F=C_{load}/C_{in}$). Multiplying F,G and B gave us path effort H ($H=F \cdot G \cdot B$). Including the levels contributed by each gates within the Black and Gray Cells, we figured out that there are total N=10 stages, which in turn gave us the value 'h' which is the optimum stage effort ($h^N=H$). Working backward from the Buffer at the C_{out} stage, we figure out the sizing of gates and individual CMOS ratios for each stage along the critical path. This sizing of the gates is only along the critical path as we have used minimum sized gates and buffers on the path other than the critical path. This sizing was done keeping in mind the load of 100f Farad which gave us a 67.49 ps Rise time and 64 ps Fall time.

However, since the post-layout simulation was only for a load of 10f Farad, we have used minimum sized elements along the critical path and only the buffer at the output is sized. This decision was taken since minimum sized elements were enough in driving the 10f Farad Load.

The speciality of our design is that we have managed to fulfill the timing requirements, delivering a fast-computing adder while also managing to use limited area for the layout.

D. Layout

We started the layout design, buy planning the transistor placement of each separate cell. This is called stick-diagrams, but it was not exactly the same style as visible on figure 5. The program used is PowerPoint.

 


Fig.5: Layout planning of Xor gate

Although all the cells are planned, the actual layout had to follow the drc rules. We tried not to use metal 2 layer in these cells, but for more complicated cells it was inevitable.

 


Fig.6: Actual layout of XOR gate.

The height of the cells were increased to 1.380 micrometer, to have space for increased sized activate areas, which in the end design we didn't use, as it was not a 100fF design. This increased height still helped with the routing.

 


Fig.7: Layout of the adder.

For the final design, we placed in all the cells, so that their VDD and GND metall rails are in the same position, as shown in the lab videos. Every second line is rotated for matching rails. The biggest cells were pg_logic, the longest line is still the buffer part. The design is not perfect, better placement of the cells would have been possible. The constraint is simply time and complexity, as it is very difficult to see which component is which, if the cells are not keeping the same lines as in the schematic. Overall we spent more than 60 hours on completing the layout after all the separate cells were done, which also took considerable amount of effort. The wiring tool in layout design would have been a great help if explained earlier, and would have been save us much time, sadly we only found out about it halfway through. (ctrl+shift+w in layout design). Figure 7 shows the effort of routing, which was the most difficult in the congested grey cell / black cell area as those cells have 4/6 connections in a smaller area. Metal 2, 3, 4, and also 5 was used. After layer 4 it becomes increasingly difficult to find enough space for the vias, as metal 4 already needs spacing of 140nm.

3. J. Sklansky, "Conditional-Sum Addition Logic," in *IRE Transactions on Electronic Computers*, vol. EC-9, no. 2, pp. 226-231, June 1960.